



ESc201, Lecture 8: Sinusoidal steady state analysis

Phasor algebra :

$$v(t) = 3 \cos(\omega t + 45^\circ) \iff 3 \angle 45^\circ \iff 3 \cos(45^\circ) + j3 \sin(45^\circ)$$

$$5 \angle -60^\circ \iff v(t) = 5 \cos(\omega t - 60^\circ)$$

Let $v_1(t) = 5\cos(\omega t + \pi/6)$ and $v_2(t) = 10\cos(\omega t - \pi/4)$

Since both signals have the same frequency and both are in *cosine representation*

Phasor algebra can be performed on them i.e.

$$\text{V}_1(j\omega) = 5 \angle 30^\circ = 5\cos 30^\circ + j5\sin 30^\circ = 4.33 + j2.5$$

$$\text{V}_2(j\omega) = 10 \angle -45^\circ = 10\cos 45^\circ - j10\sin 45^\circ = 7.07 - j7.07$$

$$v_1(t) + v_2(t) = \text{V}_1(j\omega) + \text{V}_2(j\omega) = 4.33 + j2.5 + 7.07 - j7.07 \\ = 11.41 - j4.57 = (11.41^2 + 4.57^2)^{1/2} \angle \tan^{-1}(-4.57/11.41) = 12.29 \angle 22.83^\circ.$$

$$(a + jb)/(x + jy) = (a + jb)(x - jy) / (x^2 + y^2) = [(ax + by) + j(bx - ay)] / (x^2 + y^2)$$

$$\text{OR } [\sqrt{a^2 + b^2}] \angle \tan^{-1}(b/a) / [\sqrt{x^2 + y^2}] \angle -\tan^{-1}(y/x)$$

$$= [\sqrt{(a^2 + b^2) / (x^2 + y^2)}] \angle \{\tan^{-1}(b/a) - [-\tan^{-1}(y/x)]\}$$

$$= K \cos\{\tan^{-1}(b/a) + \tan^{-1}(y/x)\} + jK \sin\{\tan^{-1}(b/a) - [-\tan^{-1}(y/x)]\}$$


Remember Impedances are written as :

$$\frac{\text{V}_R}{\text{I}_R} = R \quad \frac{\text{V}_C}{\text{I}_C} = \frac{1}{j\omega C} = -j \left(\frac{1}{\omega C} \right) = -jX_C \quad \frac{\text{V}_L}{\text{I}_L} = j\omega L = jX_L$$

Admitances are written as : $(1/R) = G$, $j\omega C = j(1/X_C)$, and $-j(1/\omega L) = -j(1/X_L)$



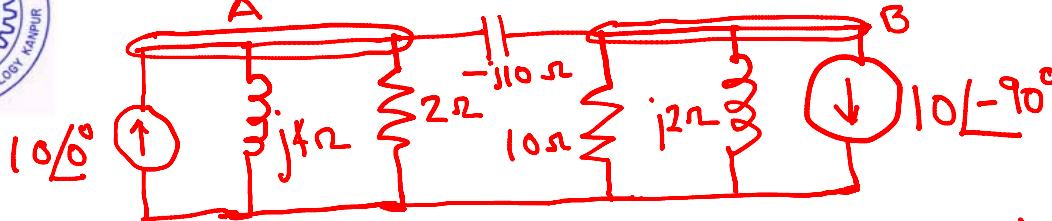ESc201, Lecture 8: Sinusoidal steady state analysis



Find V_A & V_B by
node~~at~~ Analysis

KCL at node A

$$10\angle 0^\circ = \frac{V_A}{j4} + \frac{V_A}{2} + \frac{V_A - V_B}{-j10}$$

$$\begin{aligned} \text{or } 10 &= (0.5 - j0.25 + j0.1)V_A - j0.1V_B \\ &= (0.5 - j0.15)V_A - j0.1V_B \end{aligned}$$

$$\begin{aligned} 10 &= (0.5 - j0.15)V_A \\ &\quad - (i-4)(i0.1) - j0.1V_A(-0.01 - j0.04) \end{aligned}$$

$$\therefore 1.7 = (0.85 - j0.025)V_A + 0.1 + j0.4 - (0.004 - 0.001j)V_A$$

$$\text{or } 1.6 - j0.4 = (0.846 - j0.0245)V_A$$

$$1.65 \angle -14^\circ = 0.846 \angle -1.66^\circ V_A$$

$$\therefore V_A = 1.95 \angle -12.34^\circ = 1.9 - j0.417 V$$

KCL at node B

$$\frac{V_B - V_A}{-j10} + \frac{V_B}{10} + \frac{V_B}{j2} + 10(0 - i) = 0$$

$$\text{or } -j0.1V_A + (j0.1 + 0.1 - j0.5)V_B - j10 = 0$$


$$\begin{aligned} \text{or } V_B &= \frac{(j10 + j0.1V_A)(0.1 + j0.4)}{(0.1 - j0.4)(0.1 + j0.4)} \\ &= j(1 + j0.01V_A + i4 - 0.04V_A) \end{aligned}$$

$$V_B = \frac{(-4+i) \frac{0.17}{0.17} - (0.01 + 0.04)V_A}{0.17}$$

$$V_B = \frac{9.12 \angle 3^\circ}{0.1 \angle 90^\circ} = 91.2 \angle 93^\circ = -4.77 + j91 V$$



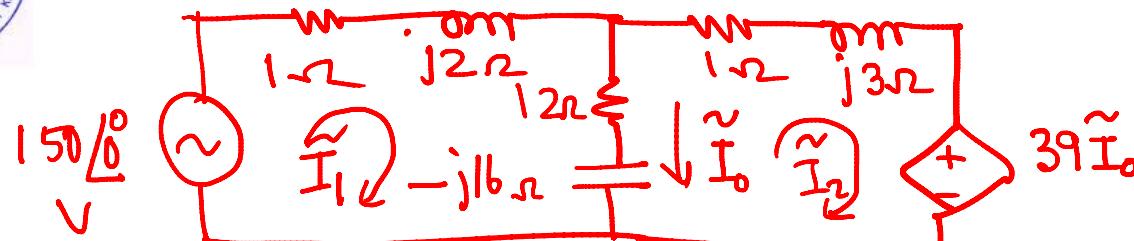ESc201, Lecture 8: Sinusoidal steady state analysis



$$\text{Loop 1: } 150 = (1+j2)\tilde{I}_1 + (12-j16)(\tilde{I}_1 - \tilde{I}_2) \rightarrow 150 = (13-j14)\tilde{I}_1 - (12-j16)\tilde{I}_2$$

$$\text{Loop 2: } 0 = (12-j16)(\tilde{I}_2 - \tilde{I}_1) + (1+j3)\tilde{I}_2 + 39\tilde{I}_0. \quad \tilde{I}_0 = \tilde{I}_1 - \tilde{I}_2$$

$$0 = (27+j16)\tilde{I}_1 - (26+j13)\tilde{I}_2 \quad \leftarrow \dots \text{ (1)}$$

$$\text{So } (27+j16)\tilde{I}_1 = (26+j13)\tilde{I}_2 \text{ or } \tilde{I}_2 = \left(\frac{27+j16}{26+j13} \right) \tilde{I}_1 \quad \text{(2)}$$

$$150 = (13-j14)\tilde{I}_1 - \frac{(12-j16)(27+j16)}{(26+j13)}\tilde{I}_1 - \frac{20 \angle -53.1^\circ \times 31.4 \angle 30.7^\circ}{29 \angle 26.6^\circ} \tilde{I}_1$$


$$\tilde{I}_0 = -1.8 + j7 \text{ A}$$

$$- 21.66 \angle -49^\circ$$

$$150 = [-1.2 + 2.35j] \tilde{I}_1 \Rightarrow \tilde{I}_1 = 56.82 \angle -117^\circ * \\ \tilde{I}_2 = -24 - j58 \text{ A} = -25.8 - 51j \text{ A}$$



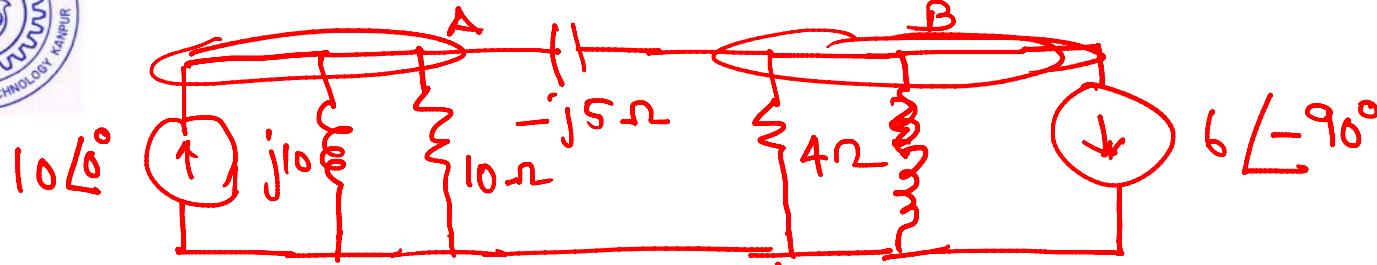
ESc201, Lecture 8: Sinusoidal steady state analysis



$$V_A \text{ and } V_B = ?$$

$$z_{eq,1} = \frac{j10 \times 10}{10 + j10} = \cancel{\frac{14 \cdot 14}{14}} \cancel{j45} = 10 + j10$$
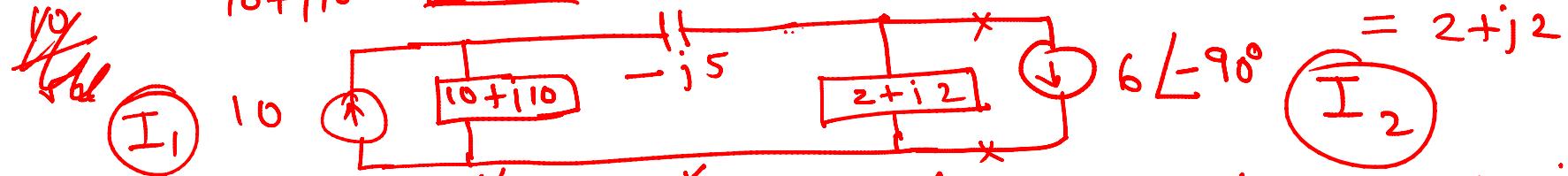
$$z_{eq,2} = \frac{j2 \times 4}{4 + j4} = \frac{4j}{1+j} = \frac{4 \angle 90^\circ}{\sqrt{2} \angle 45^\circ} = 2\sqrt{2} \angle 45^\circ$$




$$141.4 \angle 45^\circ = \frac{141 \cdot 4 \angle 45^\circ}{10 + j10 - j5 + 2 + j2} \times (2 + j2)$$

$$\sqrt{B} = \frac{141 \cdot 4 \angle 45^\circ}{10 + j10 - j5 + 2 + j2} \times (2 + j2)$$

$$V_A' = \frac{141 \cdot 4 \angle 45^\circ}{10 + j10 - j5 + 2 + j2} \times (2 + j2 - j5)$$
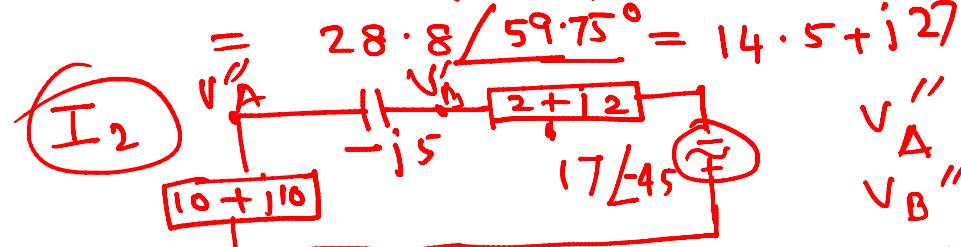
$$= 36 \cdot 6 \angle -41.55^\circ = 27 \cdot 4 - j24.3$$



$$V_A'' = -17 \cdot 3 \angle 30.25^\circ = -14.94 + j8.715$$


$$V_B'' = -13 \cdot 6.7 \angle 48.65^\circ = -12.5 - j15.6$$

$$V_A = V_A' + V_A'' \quad V_B = V_B' + V_B''$$

$$V_A = 12.5 - j15.6 \quad , \quad V_B = 5.5 - j37.26$$




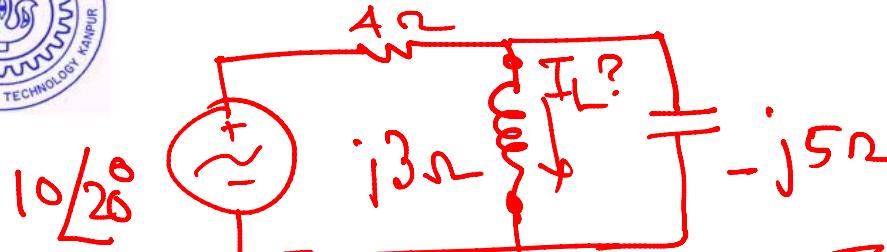
ESc201, Lecture 8: Sinusoidal steady state analysis



$$V_{Th} = \frac{10 \angle 20^\circ (-j5)}{4 + (-j5)}$$

$$= \frac{10 \angle 20^\circ \times 5 \angle -90^\circ}{6.4 \angle -51.34^\circ}$$

$$= 7.81 \angle -19^\circ$$

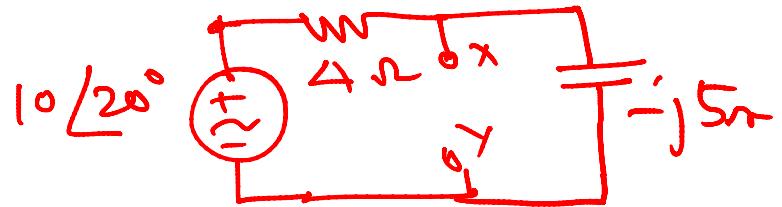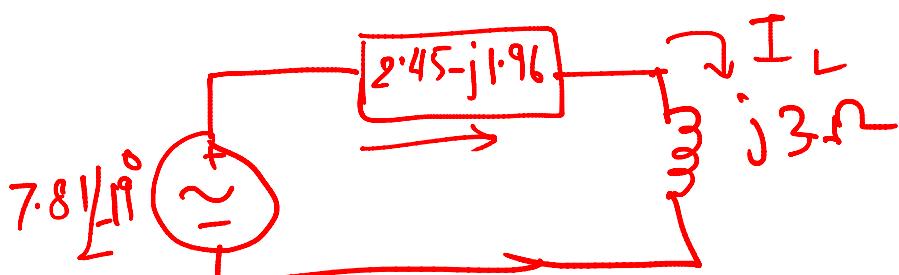

$$Z_{Th} = 4\Omega \parallel -j5\Omega$$

$$= \frac{4 \times (-j5)}{4 + (-j5)} = \frac{-20j}{4-j5} = \frac{20 \angle 90^\circ}{6.4 \angle 51.34^\circ}$$

$$= 3.14 \angle -38.66^\circ = 2.45 - j1.96 \Omega$$

$$I_L = \frac{7.81 \angle -19^\circ}{2.45 - j1.96 + j3}$$

$$= \frac{7.81 \angle -19^\circ}{2.66 \angle 23^\circ}$$

$$= 2.94 \angle -42^\circ$$

$$= 2.18 - j1.97 \text{ A}$$